





CIRCUIT THEORY I

Assoc. Prof. Hulusi Açıkgöz

Lecture 4: The node-voltage and the mesh-current methods for circuit analysis.

TERMINOLOGY

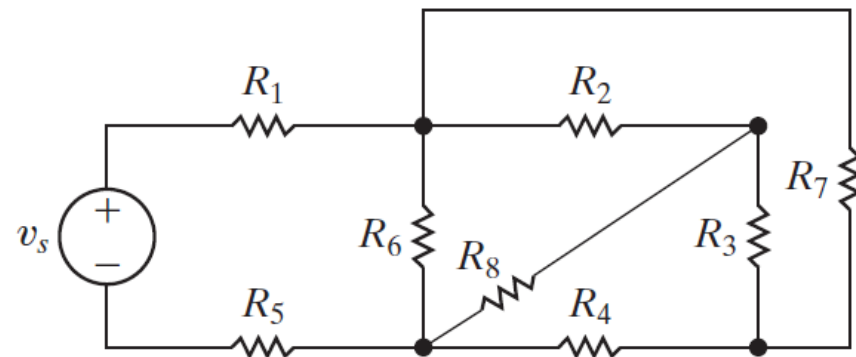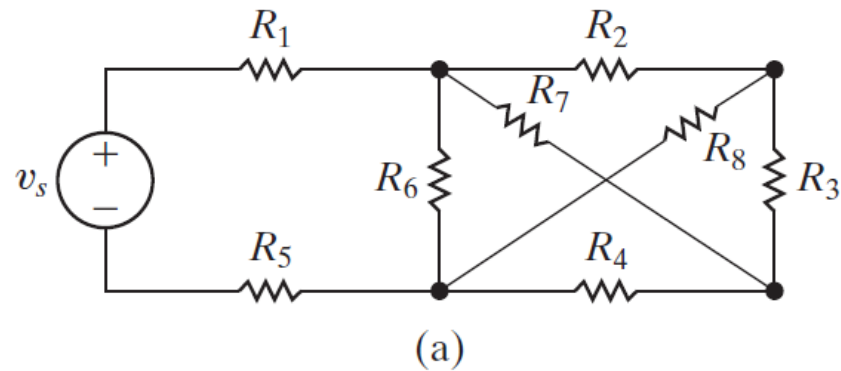
Those circuits that can be drawn on a plane with no crossing branches.



(a) A planar circuit. (b) The same circuit redrawn to verify that it is planar.

TERMINOLOGY

A nonplanar circuit

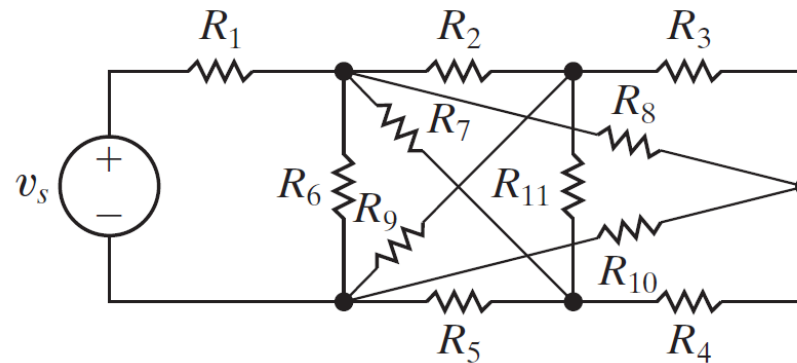

a nonplanar circuit cannot be redrawn in such a way that all the node connections are maintained and no branches overlap.


The node-voltage method is applicable to both planar and nonplanar circuits, **whereas the mesh-current method is limited to planar circuits.**

TERMINOLOGY

Name	Definition
node	A point where two or more circuit elements join
essential node	A node where three or more circuit elements join
path	A trace of adjoining basic elements with no elements included more than once
branch	A path that connects two nodes
essential branch	A path which connects two essential nodes without passing through an essential node
loop	A path whose last node is the same as the starting node
mesh	A loop that does not enclose any other loops
planar circuit	A circuit that can be drawn on a plane with no crossing branches

TERMINOLOGY

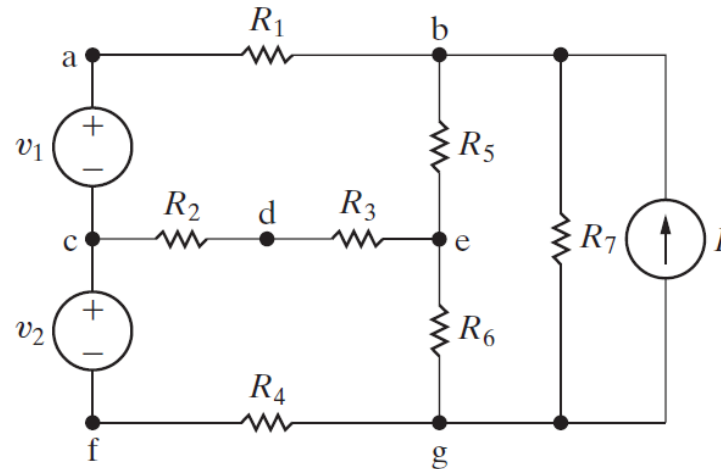Example: Identifying Node, Branch, Mesh and Loop in a Circuit




For the circuit in Figure, identify

- a) all nodes. b) all essential nodes.
- c) all branches. d) all essential branches.
- e) all meshes. f) two paths that are not loops or essential branches.
- g) two loops that are not meshes.

TERMINOLOGY


Solution:

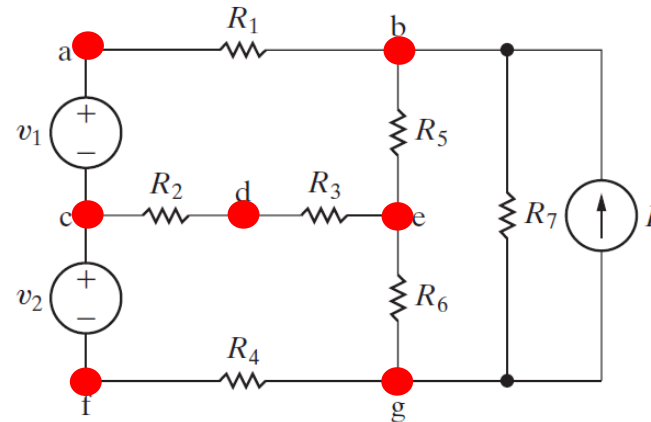

- a) The nodes are a, b, c, d, e, f, and g.
- b) The essential nodes are b, c, e, and g.
- c) The branches are v_1 , v_2 , R_1 , R_2 , R_3 , R_7 , and I .

TERMINOLOGY


Solution:

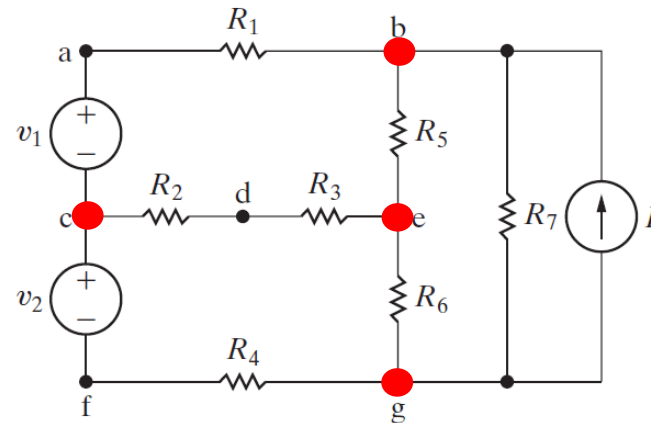

- a) The nodes are a, b, c, d, e, f, and g.
- b) The essential nodes are b, c, e, and g.
- c) The branches are v_1 , v_2 , R_1 , R_2 , R_3 , R_7 , and I .

TERMINOLOGY

Solution:

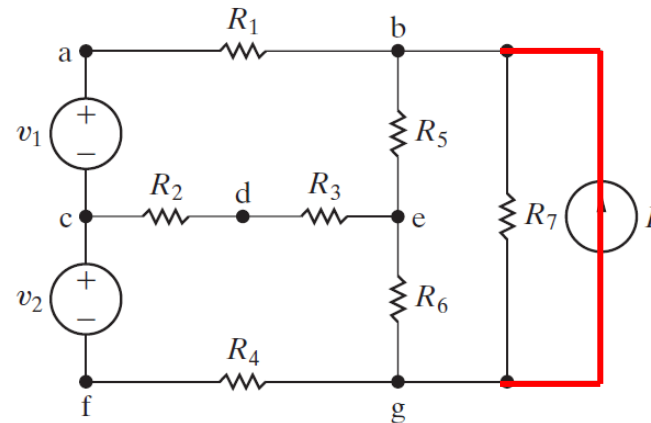

- a)** The nodes are a, b, c, d, e, f, and g.
- b)** The essential nodes are b, c, e, and g.
- c)** The branches are v_1 , v_2 , R_1 , R_2 , R_3 , R_7 , and I .

TERMINOLOGY

d) The essential branches are $v_1 - R_1$, $R_2 - R_3$, $v_2 - R_4$, R_5 , R_6 , R_7 and I

e) The meshes are $v_1 - R_1 - R_5 - R_3 - R_2$,
 $v_2 - R_2 - R_3 - R_6 - R_4$, $R_5 - R_7 - R_6$,
 and $R_7 - I$.


f) $R_1 - R_5 - R_6$ is a path, but it is not a loop

(because it does not have the same starting and ending nodes), nor is it an essential branch

(because it does not connect two essential nodes). $v_2 - R_2$ is also a path but is neither a loop nor an essential branch, for the same reasons.

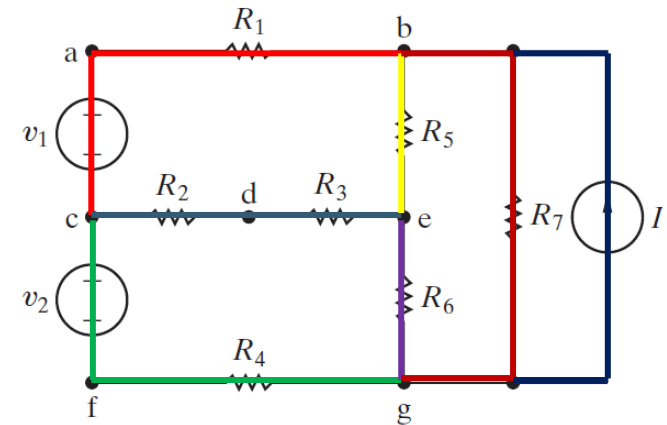g) $v_1 - R_1 - R_5 - R_6 - R_4 - v_2$ is a loop but is not a mesh, because there are two loops within it.

$I - R_5 - R_6$ is also a loop but not a mesh.



TERMINOLOGY

d) The essential branches are $v_1 - R_1$, $R_2 - R_3$, $v_2 - R_4$, R_5 , R_6 , R_7 and I

e) The meshes are $v_1 - R_1 - R_5 - R_3 - R_2$,

$v_2 - R_2 - R_3 - R_6 - R_4$, $R_5 - R_7 - R_6$,

and $R_7 - I$.


f) $R_1 - R_5 - R_6$ is a path, but it is not a loop

(because it does not have the same starting and ending nodes), nor is it an essential branch

(because it does not connect two essential nodes). $v_2 - R_2$ is also a path but is neither a loop nor an essential branch, for the same reasons.

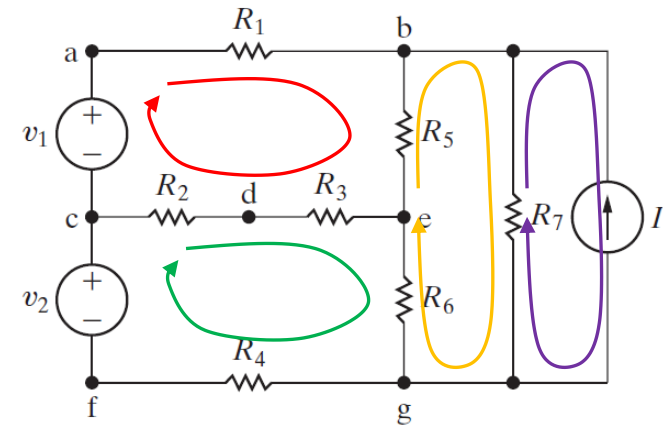g) $v_1 - R_1 - R_5 - R_6 - R_4 - v_2$ is a loop but is not a mesh, because there are two loops within it.

$I - R_5 - R_6$ is also a loop but not a mesh.



TERMINOLOGY

d) The essential branches are $v_1 - R_1$, $R_2 - R_3$, $v_2 - R_4$, R_5 , R_6 , R_7 and I

e) The meshes are $v_1 - R_1 - R_5 - R_3 - R_2$,

$v_2 - R_2 - R_3 - R_6 - R_4$, $R_5 - R_7 - R_6$,

and $R_7 - I$.


f) $R_1 - R_5 - R_6$ is a path, but it is not a loop

(because it does not have the same starting and ending nodes), nor is it an essential branch

(because it does not connect two essential nodes). $v_2 - R_2$ is also a path but is neither a loop nor an essential branch, for the same reasons.

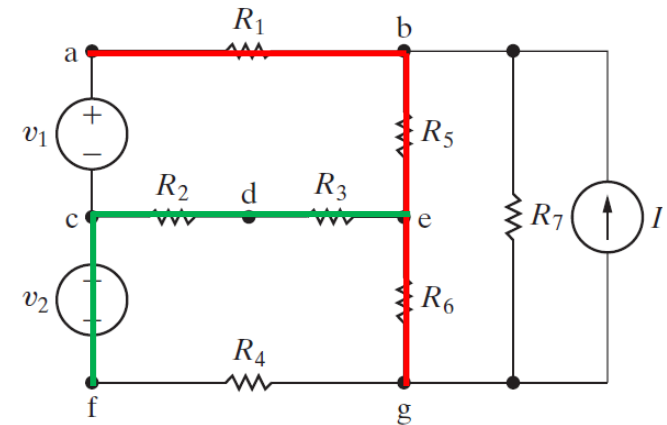g) $v_1 - R_1 - R_5 - R_6 - R_4 - v_2$ is a loop but is not a mesh, because there are two loops within it.

$I - R_5 - R_6$ is also a loop but not a mesh.



TERMINOLOGY

d) The essential branches are $v_1 - R_1$, $R_2 - R_3$, $v_2 - R_4$, R_5 , R_6 , R_7 and I

e) The meshes are $v_1 - R_1 - R_5 - R_3 - R_2$,

$v_2 - R_2 - R_3 - R_6 - R_4$, $R_5 - R_7 - R_6$,

and $R_7 - I$.


f) $R_1 - R_5 - R_6$ is a path, but it is not a loop

(because it does not have the same starting and ending nodes), nor is it an essential branch


(because it does not connect two essential nodes). $v_2 - R_2$ is also a path but is neither a loop nor an essential branch, for the same reasons.

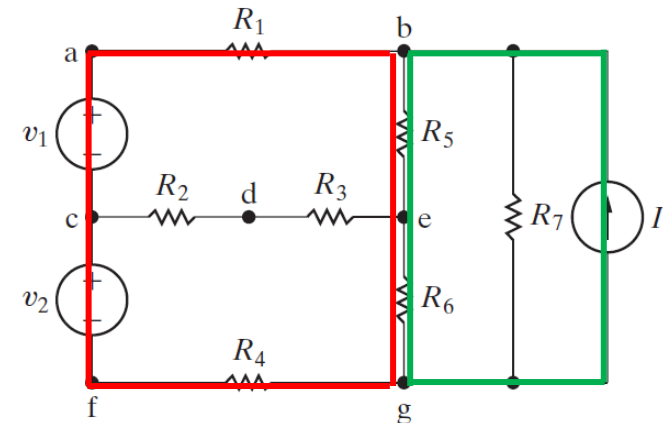g) $v_1 - R_1 - R_5 - R_6 - R_4 - v_2$ is a loop but is not a mesh, because there are two loops within it.

$I - R_5 - R_6$ is also a loop but not a mesh.



TERMINOLOGY

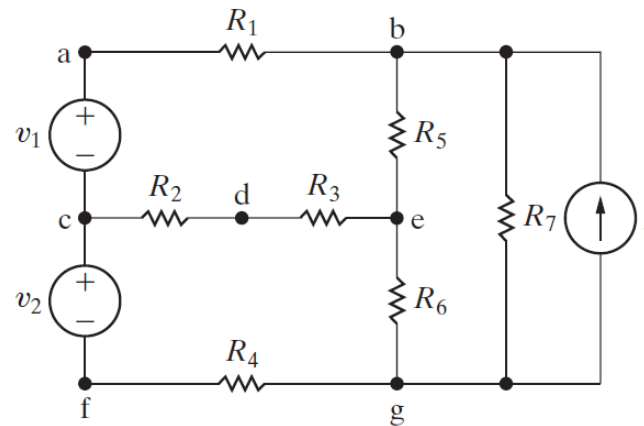

node

A point where two or more circuit elements join

a

essential node

A node where three or more circuit elements join

b

path

A trace of adjoining basic elements with no elements included more than once

$v_1 - R_1 - R_5 - R_6$

branch

A path that connects two nodes

R_1

essential branch

A path which connects two essential nodes without passing through an essential node

$v_1 - R_1$

loop

A path whose last node is the same as the starting node

$v_1 - R_1 - R_5 - R_6 - R_4 - v_2$

mesh

A loop that does not enclose any other loops


$v_1 - R_1 - R_5 - R_3 - R_2$

NODE-VOLTAGE METHOD

In this method, first we select the reference node, i.e., the ground node, and then determine other nodes.


Then, we write the KCL equations for each node in terms of voltages and solve the equation set and determine all the voltages and currents.

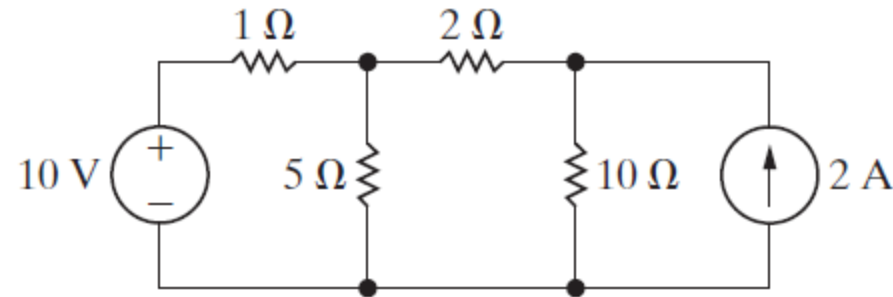Example: Analysis the circuit below using node-voltage method.




NODE-VOLTAGE METHOD

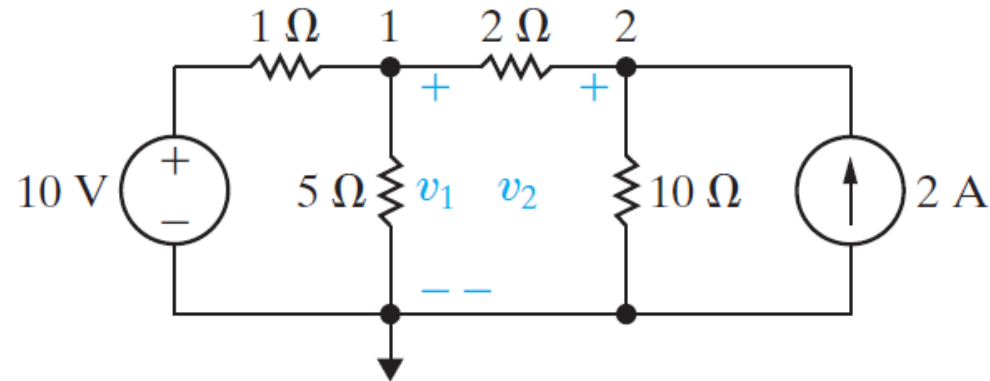Solution: We label the nodes and indicate the reference node as in



The currents for node-1 is shown below

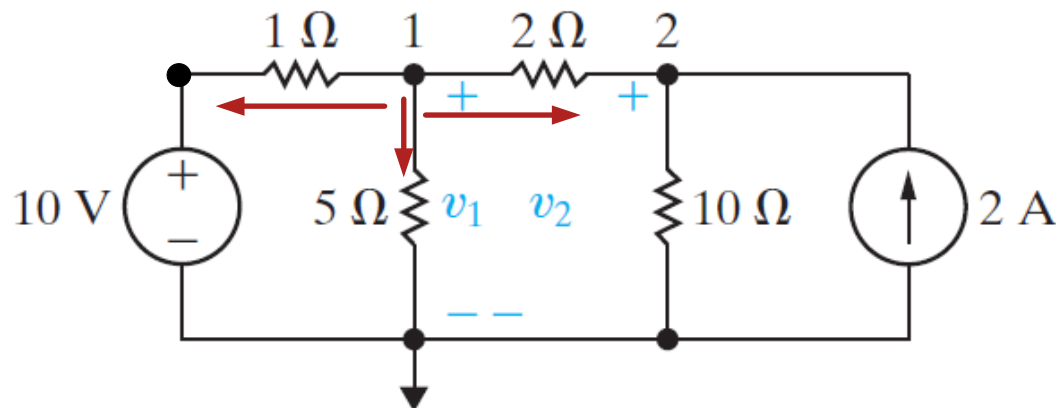


KCL at node-1 gives

$$\frac{v_1 - 10}{1} + \frac{v_1}{5} + \frac{v_1 - v_2}{2} = 0 \quad (Eq1)$$

NODE-VOLTAGE METHOD

The currents for node-2 is shown below

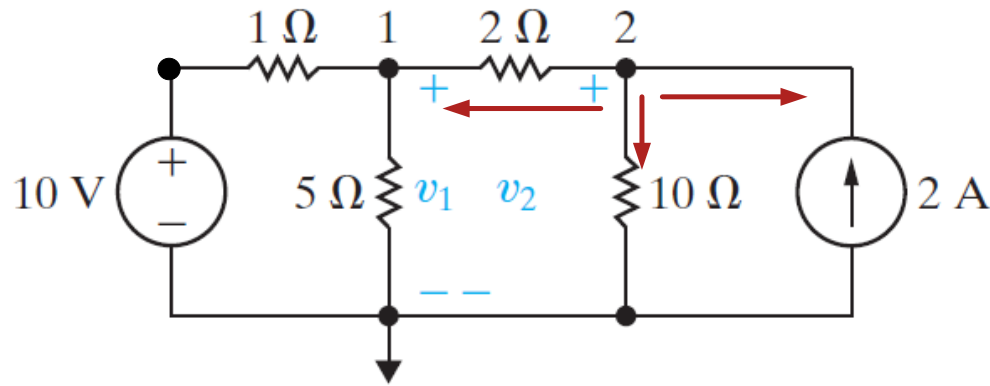

KCL at node-2 gives

$$\frac{v_2 - v_1}{2} + \frac{v_2}{10} - 2 = 0 \quad (Eq2)$$

Thus we have,

$$\frac{v_1 - 10}{1} + \frac{v_1}{5} + \frac{v_1 - v_2}{2} = 0$$

$$\frac{v_2 - v_1}{2} + \frac{v_2}{10} - 2 = 0$$


We can solve the above equation set for v_1 and v_2 and obtain

$$v_1 = 9.09 \text{ V} \quad v_2 = 10.91 \text{ V}$$

NODE-VOLTAGE METHOD

Example:

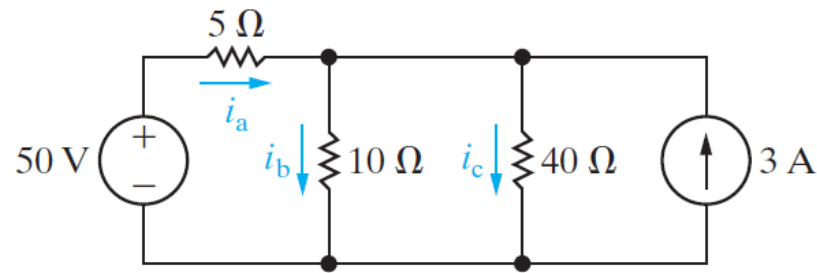- a) Use the node-voltage method of circuit analysis to find the branch currents in the circuit shown below.
- b) Find the power associated with each source, and state whether the source is delivering or absorbing power.



NODE-VOLTAGE METHOD

Solution: We label the nodes and indicate the reference node as in

KCL at node-1 gives

$$\frac{v_1 - 50}{5} + \frac{v_1}{10} + \frac{v_1}{40} - 3 = 0$$


from which we get

$$v_1 = 40 \text{ V}$$

Then, the currents are found as

$$i_a = \frac{50 - v_1}{5} = \frac{50 - 40}{5} \rightarrow i_a = 2 \text{ A} \quad i_b = \frac{v_1}{10} = \frac{40}{10} \rightarrow i_b = 4 \text{ A}$$
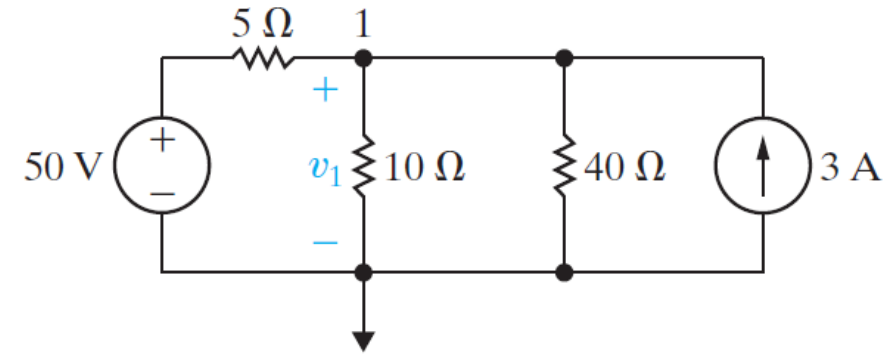
$$i_c = \frac{v_1}{40} = \frac{40}{40} \rightarrow i_c = 1 \text{ A}$$



NODE-VOLTAGE METHOD

The power associated with the 50 V source is

$$p_s = -50i_a = -100W \quad (\text{delivering})$$

The power associated with the 3A V source is


$$p_s = -40 \times 3 = -120W \quad (\text{delivering})$$

The total delivered power is

$$100 + 120 = 220W$$


The total power consumed on resistors is
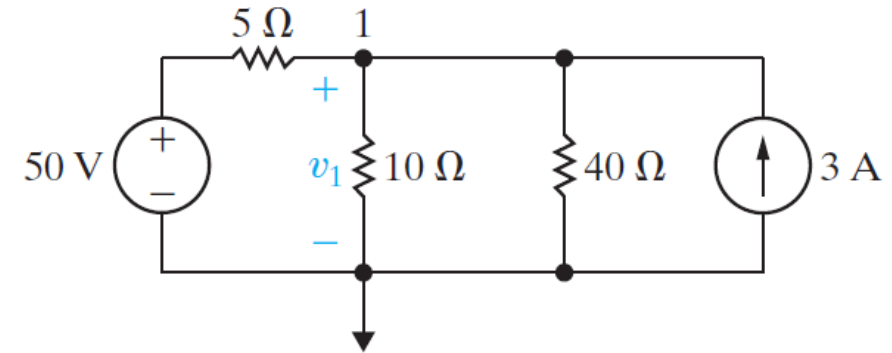
$$i_a^2 \times 5 + i_b^2 \times 10 + i_c^2 \times 40 = 220W$$



NODE-VOLTAGE METHOD

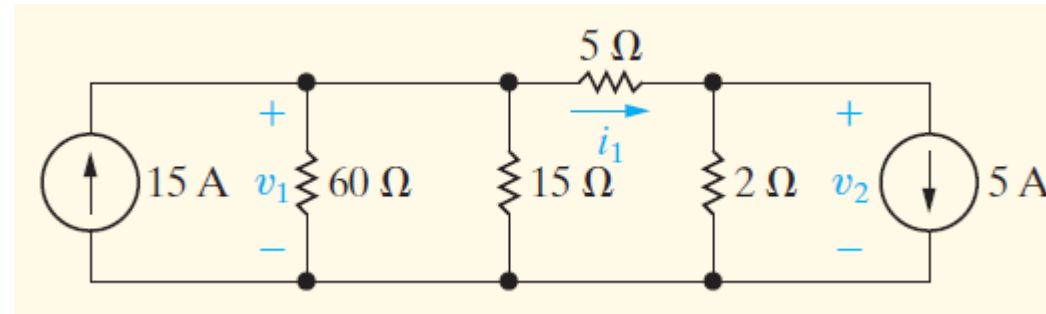Example: For the circuit shown, use the node-voltage method to find v_1 , v_2 and i_1



NODE-VOLTAGE METHOD

Solution: The nodes are labeled as in

KCL at node-1 gives

$$-15 + \frac{v_1}{60} + \frac{v_1}{15} + \frac{(v_1 - v_2)}{5} = 0 \quad (Eq1)$$

KCL at node-2 gives


$$\frac{(v_2 - v_1)}{5} + \frac{v_2}{2} + 5 = 0 \quad (Eq2)$$

These sets of equations can be solved, and we find

$$v_1 = 60 V \quad v_2 = 10V$$

The current i_1 can be calculated as
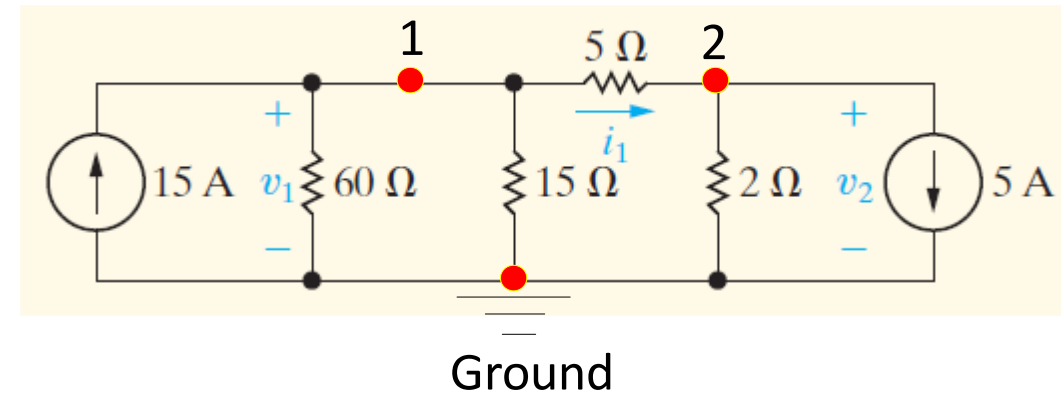
$$i_1 = \frac{v_1 - v_2}{5} \rightarrow i_1 = 10 A$$




NODE-VOLTAGE METHOD

The Node-Voltage Method and Dependent Sources

If the circuit contains dependent sources, the node-voltage equations must be supplemented with the constraint equations imposed by the presence of the dependent sources.

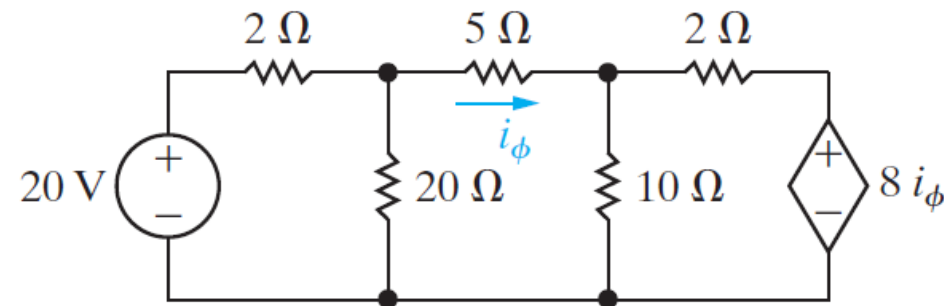Example: Use the node-voltage method to find the power dissipated in the 5Ω resistor in the circuit shown



NODE-VOLTAGE METHOD

Solution: The nodes are labeled with blue colors

From circuit we can write directly

At node-1

$$v_1 = 20 \text{ V}$$

KCL at node-2


$$\frac{v_2 - 20}{2} + \frac{v_2}{20} + \frac{v_2 - v_3}{5} = 0$$

KCL at node-3

$$\frac{(v_3 - v_2)}{5} + \frac{v_3}{10} + \frac{v_3 - v_4}{2} = 0$$

At node-4
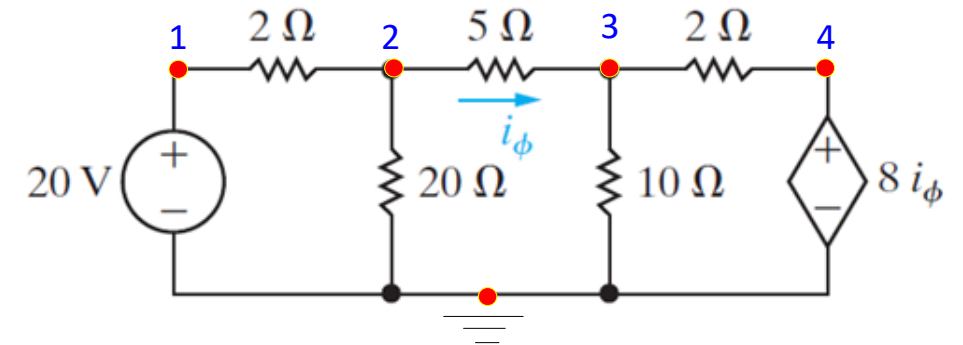
$$v_4 = 8i_\phi \quad i_\phi = \frac{(v_2 - v_3)}{5} \rightarrow v_4 = \frac{8}{5}(v_2 - v_3)$$




NODE-VOLTAGE METHOD

Solution: The nodes are labeled with blue colors

$$\frac{v_2 - 20}{2} + \frac{v_2}{20} + \frac{v_2 - v_3}{5} = 0 \quad (Eq1)$$

$$\frac{(v_3 - v_2)}{5} + \frac{v_3}{10} + \frac{v_3 - v_4}{2} = 0 \quad (Eq2)$$
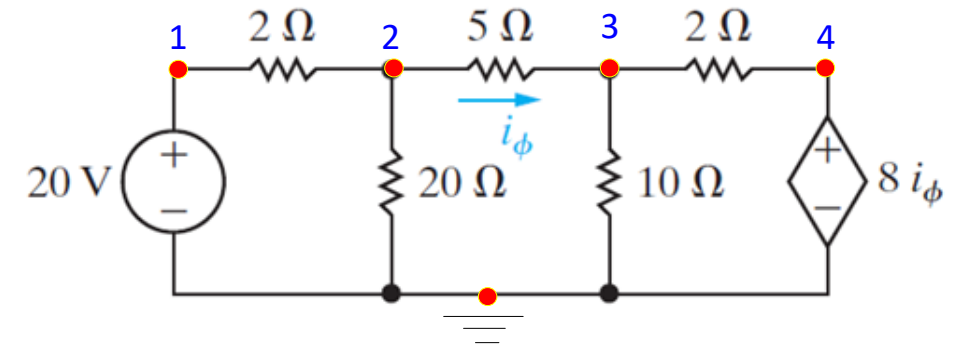
$$v_4 = \frac{8}{5}(v_2 - v_3) \quad (Eq3)$$



NODE-VOLTAGE METHOD

We can substitute $Eq3$ into $Eq2$ and we get

$$\frac{v_2 - 20}{2} + \frac{v_2}{20} + \frac{v_2 - v_3}{5} = 0 \quad (Eq1)$$

$$\frac{(v_3 - v_2)}{5} + \frac{v_3}{10} + \frac{v_3 - \frac{8}{5}(v_2 - v_3)}{2} = 0 \quad (Eq2)$$

This equation set can be solved for v_2 and v_3 and we get

$$v_2 = 16 \text{ V} \quad v_3 = 10 \text{ V}$$

The current i_ϕ is calculated as

$$i_\phi = \frac{(v_2 - v_3)}{5} \rightarrow i_\phi = \frac{16 - 10}{5} = 1.2 \text{ A}$$


The power dissipated on 5Ω resistor is

$$p = (v_2 - v_3)i_\phi \rightarrow p = 6 \times 1.2 = 7.2 \text{ W}$$

$$\frac{v_2 - 20}{2} + \frac{v_2}{20} + \frac{v_2 - v_3}{5} = 0 \quad (Eq1)$$

$$\frac{(v_3 - v_2)}{5} + \frac{v_3}{10} + \frac{v_3 - v_4}{2} = 0 \quad (Eq2)$$
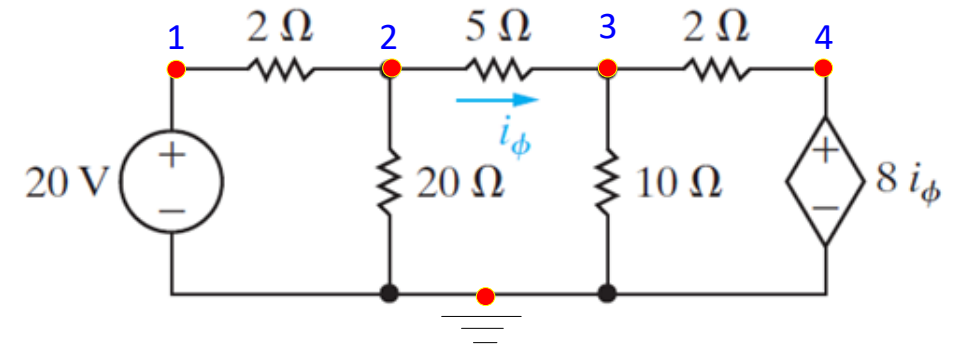
$$v_4 = \frac{8}{5}(v_2 - v_3) \quad (Eq3)$$




NODE-VOLTAGE METHOD

The Node-Voltage Method: Super Node


Note that KCL can be used **for any closed surface**, not for nodes only. A super node is formed drawing a closed surface around 2 or more nodes

We accept the closed surface as a single node. That is called super node.

Example: Consider the circuit below.

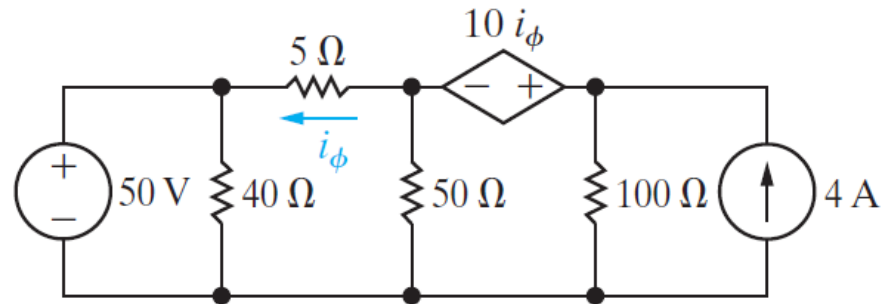


The nodes are labeled as

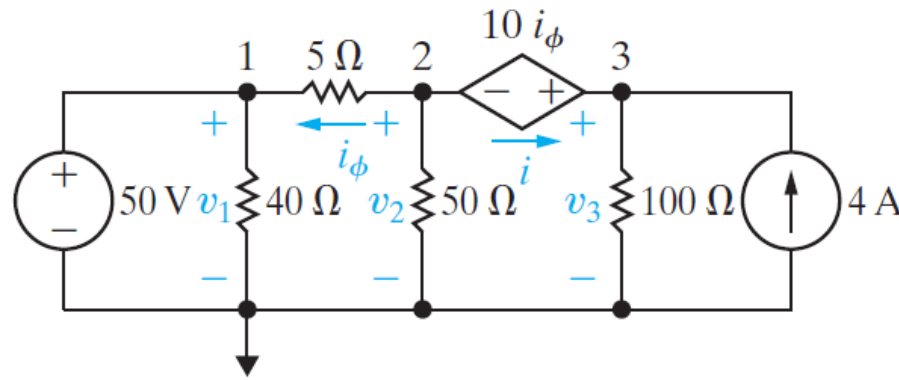

NODE-VOLTAGE METHOD

The super-node can be formed as

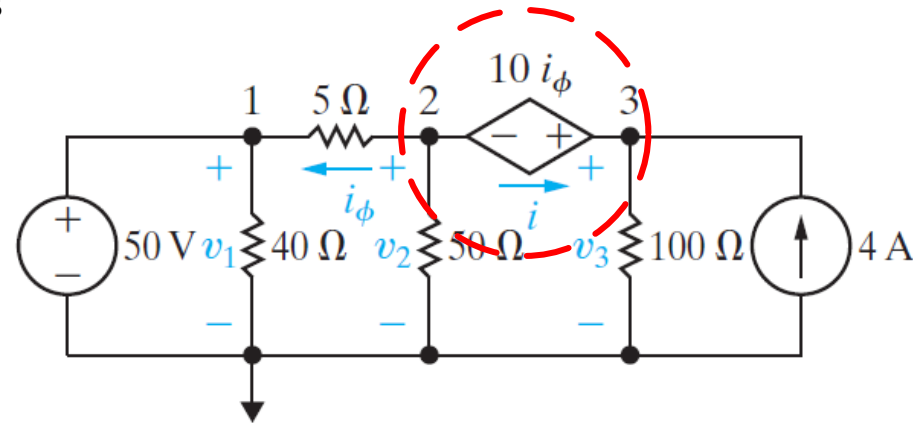

For the above circuit

$$v_1 = 50 \text{ V}$$

KCL at super-node

$$\frac{v_2 - v_1}{5} + \frac{v_2}{50} + \frac{v_3}{100} - 4 = 0 \quad (Eq1)$$

and we have

$$v_3 - v_2 = 10i_\phi \quad i_\phi = \frac{v_2 - v_1}{5}$$

NODE-VOLTAGE METHOD

Then

$$v_3 - v_2 = 10 \times \frac{v_2 - v_1}{5} \rightarrow$$

$$v_3 - v_2 = 2v_2 - 2v_1 \rightarrow$$

$$v_3 - 3v_2 + 2v_1 = 0 \quad (Eq2)$$

Thus we have


$$v_1 = 50 \text{ V}$$

$$\frac{v_2 - v_1}{5} + \frac{v_2}{50} + \frac{v_3}{100} - 4 = 0 \quad (Eq1)$$

$$v_3 - 3v_2 + 2v_1 = 0 \quad (Eq2)$$


and this equation set can be solved for v_2 and v_3 and we find that
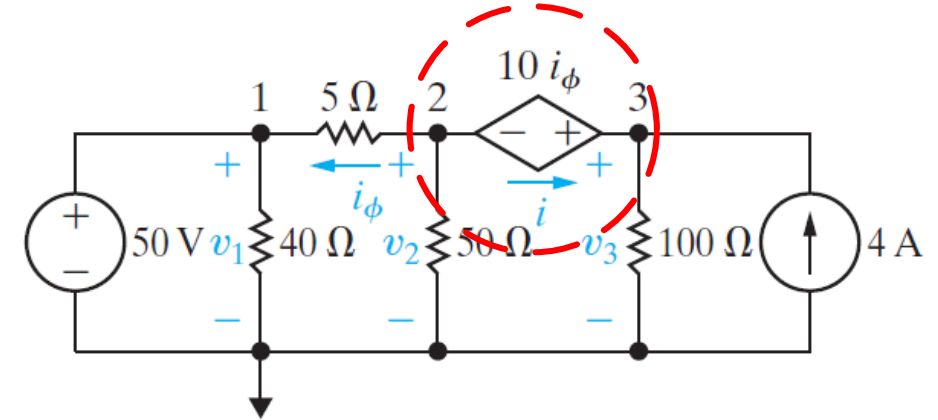
$$v_2 = 60 \text{ V} \quad v_3 = 80 \text{ V}$$




NODE-VOLTAGE METHOD

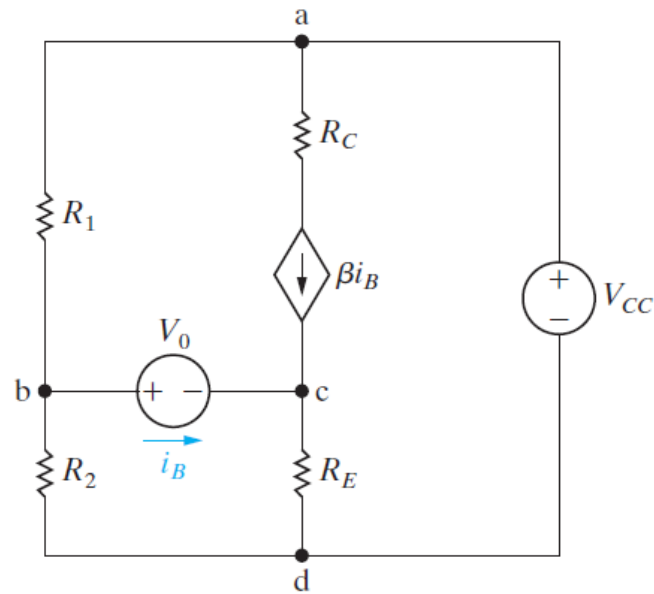Example: Find the node voltage v_b for the circuit below



NODE-VOLTAGE METHOD

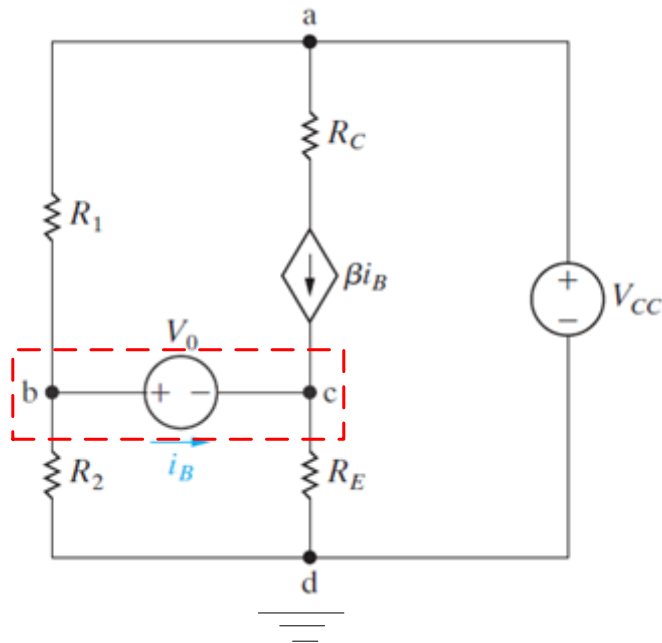Solution: The super node is shown in Figure below



$$v_a = V_{CC}$$

KCL at super node

$$\frac{v_b - v_a}{R_1} + \frac{v_b}{R_2} + \frac{v_c}{R_E} - \beta i_\beta = 0 \quad Eq1$$

And we have

$$v_c = (i_\beta + \beta i_\beta) \times R_E \quad v_b - v_c = V_0$$


from which we can write

$$v_c = v_b - V_0 \quad i_\beta = \frac{v_c}{(1 + \beta)R_E} \rightarrow i_\beta = \frac{v_b - V_0}{(1 + \beta)R_E} \quad Eq2$$

When Eq2 is used in Eq1, we get

$$\frac{v_b - V_{CC}}{R_1} + \frac{v_b}{R_2} + \frac{v_b - V_0}{R_E} - \beta \frac{v_b - V_0}{(1 + \beta)R_E} = 0$$

NODE-VOLTAGE METHOD

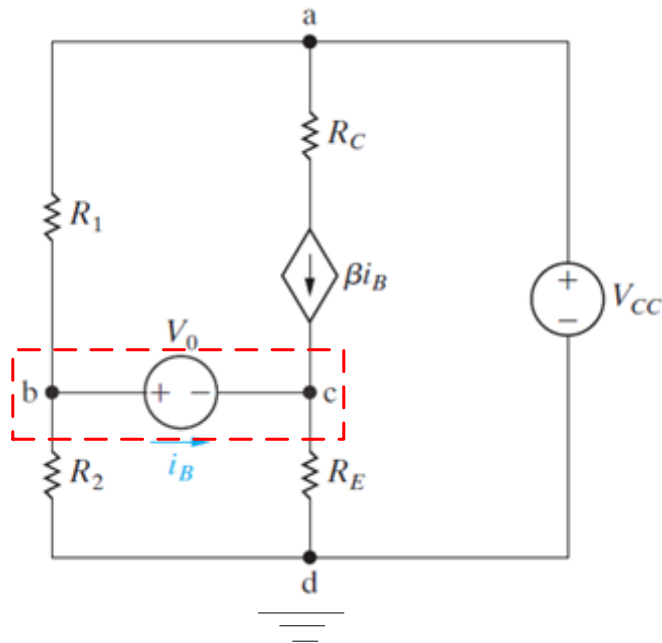

$$\frac{v_b - V_{CC}}{R_1} + \frac{v_b}{R_2} + \frac{v_b - V_0}{R_E} - \beta \frac{v_b - V_0}{(1 + \beta)R_E} = 0$$

which can be written as

$$\frac{v_b}{R_1} + \frac{v_b}{R_2} + \frac{v_b}{R_E} - \beta \frac{v_b}{(1 + \beta)R_E} = \frac{V_{CC}}{R_1} + \frac{V_0}{R_E} - \beta \frac{V_0}{(1 + \beta)R_E}$$

which is simplified as

$$\frac{v_b}{R_1} + \frac{v_b}{R_2} + \frac{v_b}{(1 + \beta)R_E} = \frac{V_{CC}}{R_1} + \frac{V_0}{(1 + \beta)R_E}$$


from which we obtain

$$v_b = \frac{V_{CC}R_2(1 + \beta)R_E + V_0R_1R_2}{R_1R_2 + (1 + \beta)R_E(R_1 + R_2)}$$

THE MESH-CURRENT METHOD

A mesh current is the current that exists only in the perimeter of a mesh. On a circuit diagram it appears as either a closed solid line or an almost-closed solid line that follows the perimeter of the appropriate mesh.

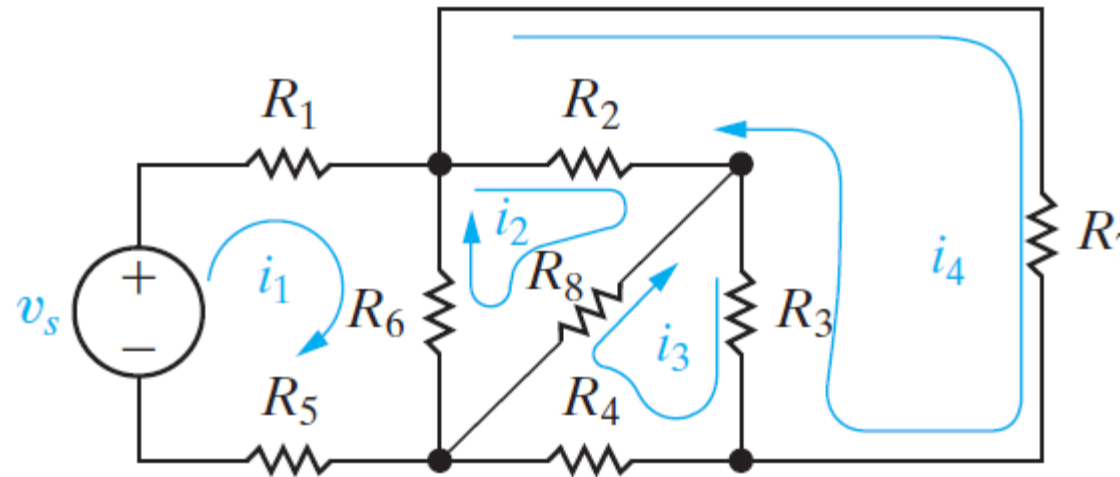
An arrowhead on the solid line indicates the reference direction for the mesh current.




Note that mesh currents are not the branch currents.

THE MESH-CURRENT METHOD

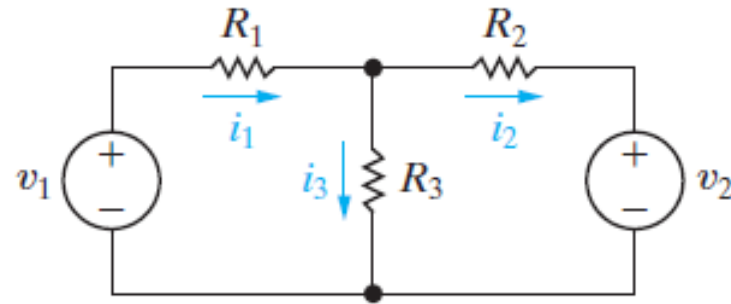Example: The branch currents are shown in the circuit below



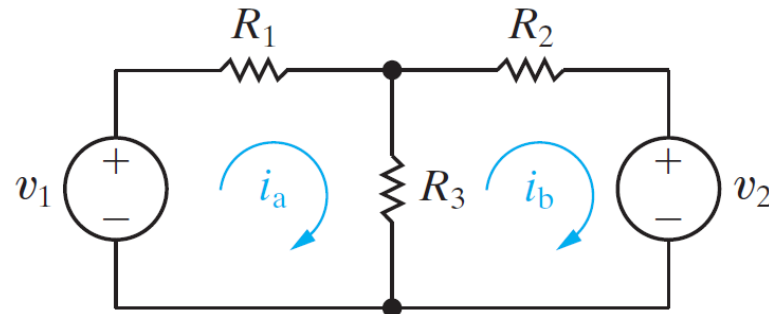The mesh currents for the above circuit is given as



The relationships between branch and mesh currents are given as

$$i_1 = i_a$$

$$i_2 = i_b$$

$$i_3 = i_a - i_b$$

THE MESH-CURRENT METHOD


The mesh equations for the below circuit are written as

KVL for the loop-a

$$-v_1 + i_a R_1 + (i_a - i_b) R_3 = 0$$

KVL for the loop-b


$$i_b R_2 + v_2 + (i_b - i_a) R_3 = 0$$

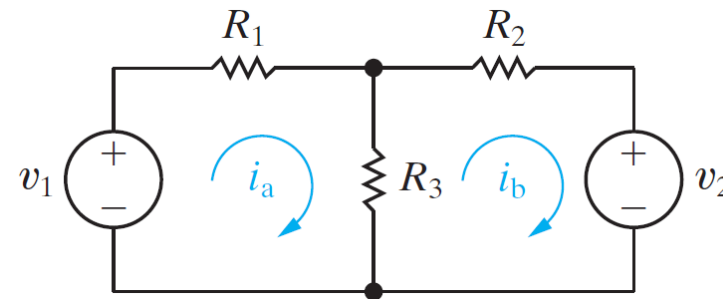

These two equations can be used to solve i_a and i_b

THE MESH-CURRENT METHOD

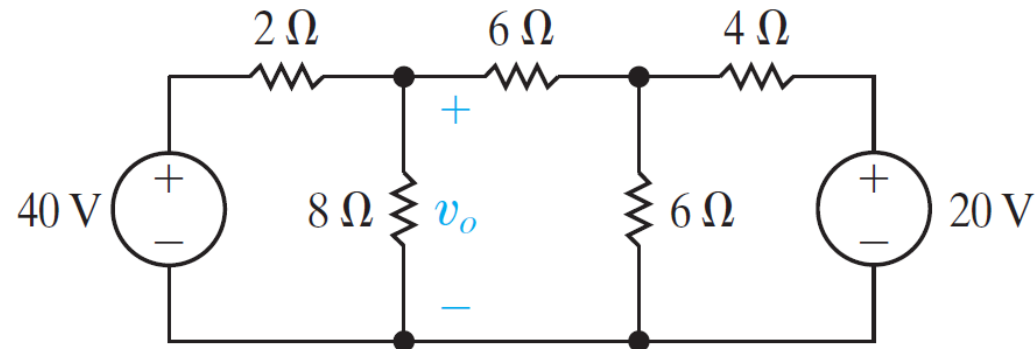Example: Use the mesh-current method to determine the power associated with each voltage source in the circuit shown in



THE MESH-CURRENT METHOD

Solution: The mesh currents are shown in the circuit

The mesh equations can be written as

Mesh-a:


$$-40 + 2i_a + 8(i_a - i_b) = 0$$

Mesh-b:

$$8(i_b - i_a) + 6i_b + 6(i_b - i_c) = 0$$

Mesh-c:

$$6(i_c - i_b) + 4i_c + 20 = 0$$

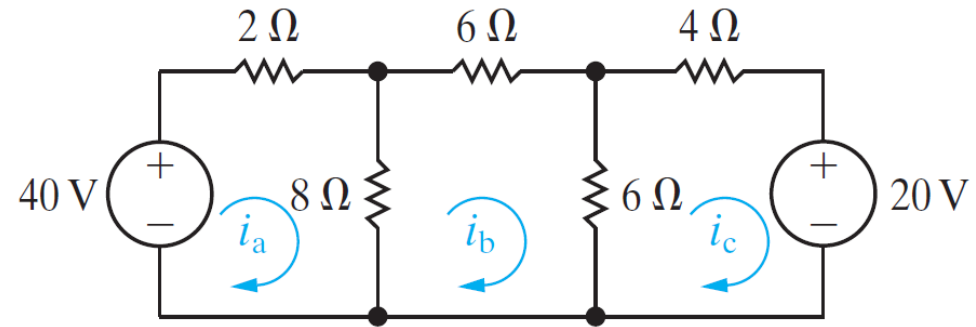

The equations can be simplified as

$$10i_a - 8i_b = 40$$

$$-8i_a + 20i_b - 6i_c = 0$$

$$-6i_b + 10i_c = -20$$

when these equations are solved, we get

$$i_a = 5.6 \text{ A}$$

$$i_b = 2.0 \text{ A}$$

$$i_c = -0.80 \text{ A}$$